
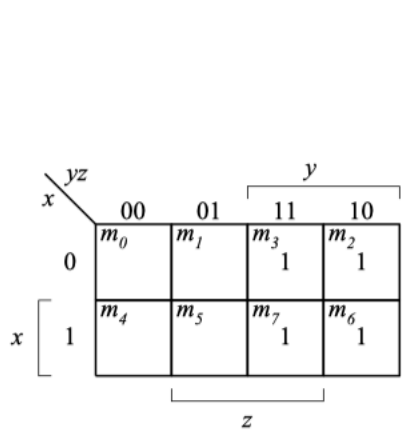


Gate-Level Minimization

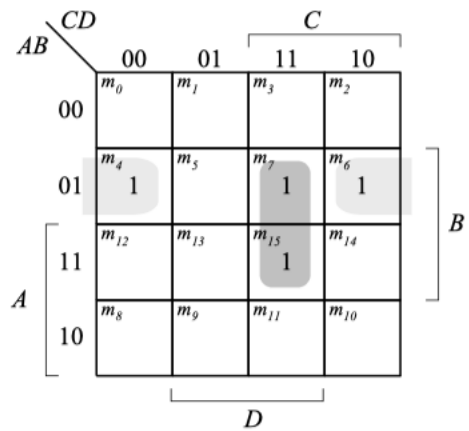
1) Simplify the following Boolean functions, using *Karnaugh* maps:




(a) $F = y$




(b) $F = BCD + A'BD'$

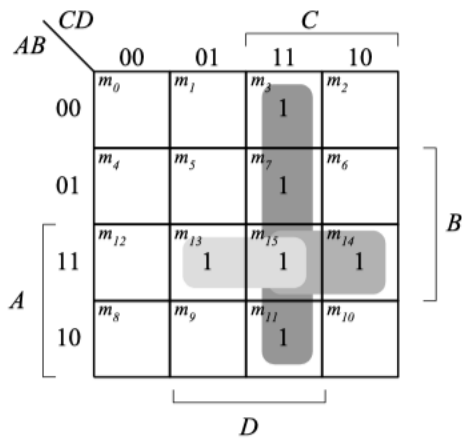

(c) $F = CD + ABD + ABC$

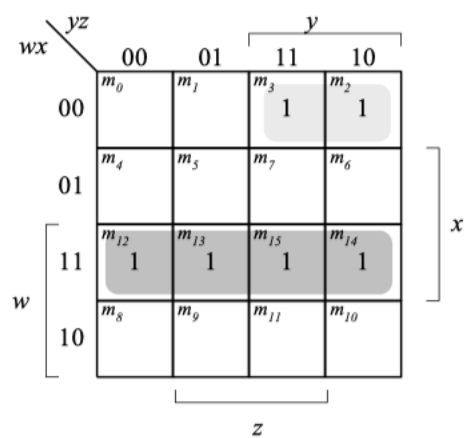


(d) $F = w'x'y + wx$

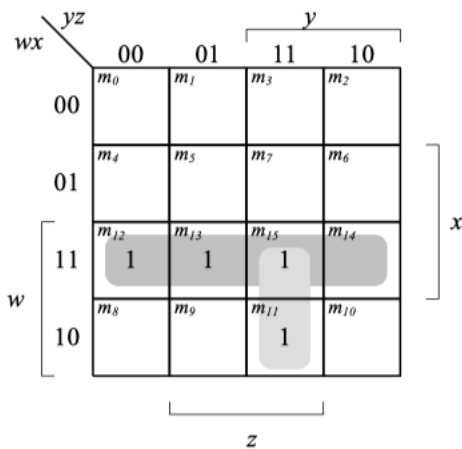

$$F = wx + wzy$$

(e)

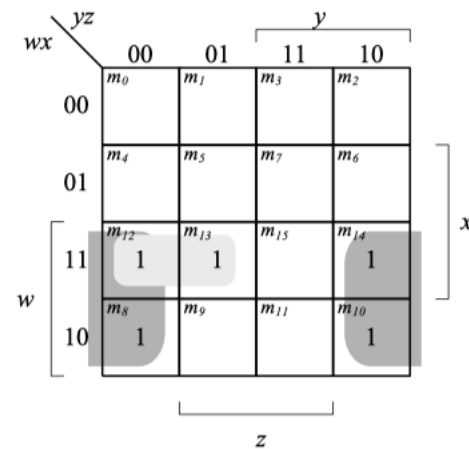

$$F = wz' + xy'w$$

(f)

2) Find the minterms of the following Boolean expressions by first plotting each function in a map:

(a) $F(x, y, z) = \Sigma(3, 5, 6, 7)$

$x \backslash yz$		y			
		00	01	11	10
x	0	m_0	m_1	1	m_2
	1	m_4	m_5	1	m_6

z

(b) $F = \Sigma(1, 3, 5, 9, 12, 13, 14)$

$AB \backslash CD$		C			
		00	01	11	10
A	00	m_0	1	1	m_2
	01	m_4	1	m_7	m_6
	11	m_{12}	1	m_{15}	1
	10	m_8	1	m_{11}	m_{10}

D

(c) $F = \Sigma(0, 1, 2, 3, 11, 12, 14, 15)$

$w \backslash x$		y			
		00	01	11	10
w	00	1	1	1	1
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	1
	10	m_8	m_9	1	m_{10}


z

(d) $F = \Sigma(3, 4, 5, 7, 11, 12)$

$AB \backslash CD$		C			
		00	01	11	10
A	00	m_0	m_1	1	m_2
	01	m_4	1	1	m_6
	11	m_{12}	1	m_{15}	m_{14}
	10	m_8	m_9	1	m_{10}

D

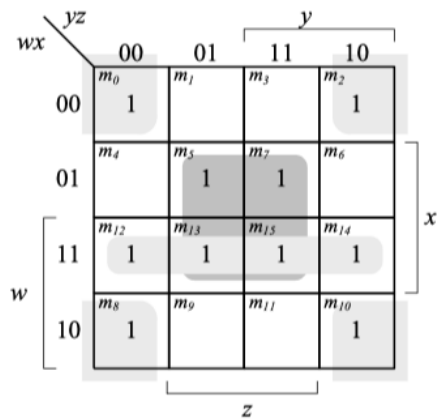- 3) Simplify the following Boolean functions by first finding the essential prime implicants:




$$F = \Sigma(0, 2, 5, 7, 8, 10, 12, 13, 14, 15)$$

Essential: $xz, wx, x'z'$

$$F = xz + wx + x'z'$$

(a)

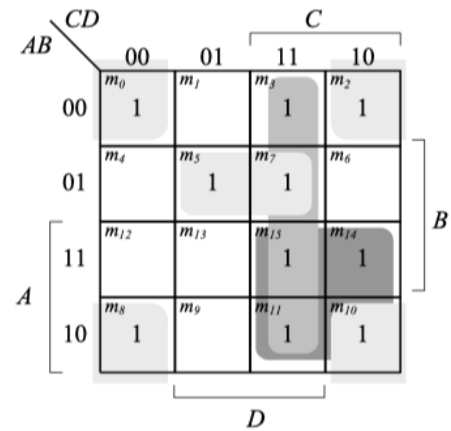


$$F = \Sigma(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$$

Essential: $AC, B'D', CD, A'BD$


$$F = AC + B'D' + CD + A'BD$$

(b)

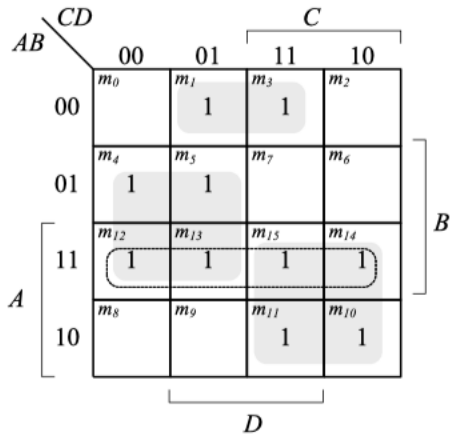


$F = \Sigma(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$
Essential: $AC, BC', A'B'D$
Non-essential: $AB, A'B'D, B'CD, A'C'D$
 $F = AC + BC' + A'B'D$

(c)

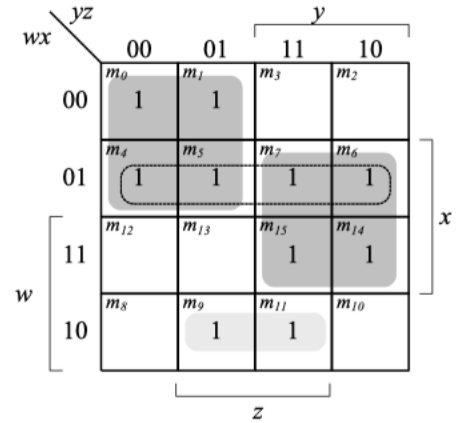


$F = \Sigma(0, 1, 4, 5, 6, 7, 9, 11, 14, 15)$
Essential: $w'y', xy, wx'z$
Non-essential: $wx, x'y'z, w'wz, w'x'z$
 $F = w'y' + xy + wx'z$

(d)

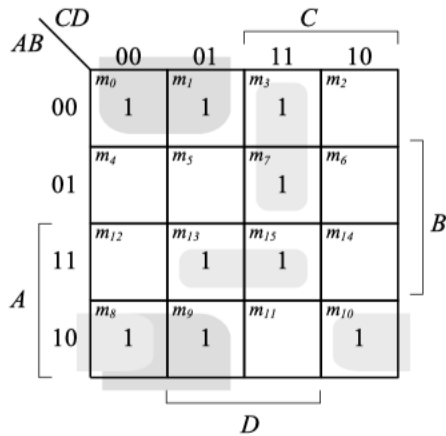

$F(A, B, C, D) = \Sigma(0, 1, 3, 7, 8, 9, 10, 13, 15)$
Essential: $B'C', AB'D'$
Non-essential: $ABD, A'CD, BCD$
 $F = B'C' + AB'D' + A'CD + ABD$

(e)

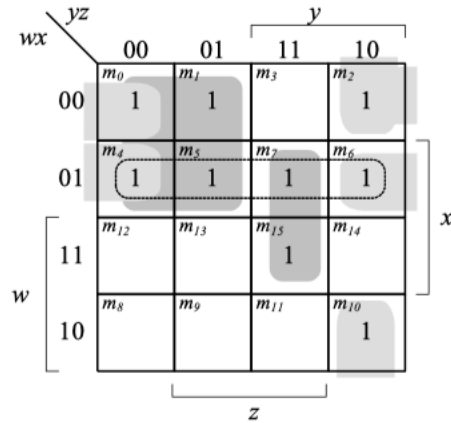

$F = \Sigma(0, 1, 2, 4, 5, 6, 7, 10, 15)$
Essential: $w'y', w'z', xyz, x'yz'$
Non-Essential: $w'x$
 $F = w'y' + w'z' + xyz + x'yz'$

(f)

4) Simplify the following expressions to (1) sum-of-products and (2) products-of-sums:

(a) $F = x'z' + y'z' + yz' + xy = x'z' + z' + xy = z' + xy$

		y			
		00	01	11	10
x	0	m ₀ 1	m ₁	m ₃	m ₂ 1
	1	m ₄ 1	m ₅	m ₇ 1	m ₆ 1

$$F' = x'z + y'z$$

$$F = (x + z')(y + z')$$

(b) $F = ACD' + C'D + AB' + ABCD$

AB		C			
		00	01	11	10
A	00	m ₀	m ₁ 1	m ₃	m ₂
	01	m ₄	m ₅ 1	m ₇	m ₆
	11	m ₁₂	m ₁₃ 1	m ₁₅ 1	m ₁₄ 1
	10	m ₈ 1	m ₉ 1	m ₁₁ 1	m ₁₀ 1

$$F = AC + AB' + C'D$$

$$F' = A'C + A'D' + BC'D'$$

$$F = (A + C')(A + D)(B' + C + D)$$

(c)

$$F = (A' + B + D')(A' + B' + C')(A' + B' + C)(B' + C + D')$$

$$F' = AB'D + ABC + ABC' + BC'D$$

		CD			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}

D

B

$$F' = AB + BC'D$$

$$F = (A' + B')(B' + C + D')$$

$$F = A'D' + A'BC + AB'$$

		CD			
		00	01	11	10
A	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}

D

B

(d)

$$F = BCD' + ABC' + ACD$$

		C				
		CD		00	01	
A	AB	00	01	11	10	B
		m_0	m_1	m_3	m_2	
	00					
	01	m_4	m_5	m_7	m_6 1	
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14}	
	10	m_8	m_9	m_{11} 1	m_{10}	
		D				

		C				
		CD		00	01	
A	AB	00	01	11	10	B
		m_0	m_1	m_3	m_2	
	00	0	0	0	0	
	01	0	0	0		
	11				0	
	10	0	0		0	
		D				

$$F' = A'C' + A'D + B'C' + A'B' + ACD'$$

$$F = (A + C)(A + D')(B + C)(A + B)(A' + C' + D)$$

- 5) Simplify the following Boolean function F , together with the don't-care conditions d , and then express the simplified function in sum-of-minterms form:

		yz		y	
		00	01	11	10
x	0	m_0 1	m_1 1	m_3 x	m_2 x
	1	m_4 1	m_5 1	m_7 x	m_6 1

z

$$F = 1$$

$$F = \Sigma(0,1, 2, 3, 4, 5, 6, 7)$$

		CD		C	
		00	01	11	10
AB	00	m_0 1	m_1	m_3	m_2 x
	01	m_4 x	m_5	m_7	m_6 1
	11	m_{12}	m_{13} 1	m_{15}	m_{14} 1
	10	m_8 1	m_9	m_{11}	m_{10} x

D

$$F = A'D' + B'D' + BCD' + ABC'D$$

$$F = \Sigma(0, 2, 4, 6, 8, 10, 13, 14)$$

		CD		C	
		00	01	11	10
AB	00	m_0	m_1	m_3 x	m_2
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12} 1	m_{13}	m_{15} 1	m_{14} 1
	10	m_8	m_9 x	m_{11} x	m_{10}

D

$$F = BC + CD + ABD' + A'BD$$

$$F = \Sigma(3, 5, 6, 7, 11, 12, 14, 15)$$

		CD		C	
		00	01	11	10
AB	00	m_0 x	m_1	m_3	m_2 1
	01	m_4 1	m_5	m_7 1	m_6 x
	11	m_{12} 1	m_{13}	m_{15}	m_{14}
	10	m_8 x	m_9	m_{11}	m_{10} 1

D

$$F = B'D' + C'D' + A'BC$$

$$F = \Sigma(0, 2, 4, 6, 7, 8, 10, 12)$$


- 6) Simplify the following functions, and implement them with two-level NAND gate circuits:

(a)



		CD				
		00	01	11	10	
AB	00	m_0 1	m_1	m_3 1	m_2 1	B
	01	m_4 1	m_5	m_7 1	m_6 1	
	11	m_{12} 1	m_{13}	m_{15} 1	m_{14} 1	
	10	m_8 1	m_9	m_{11} 1	m_{10} 1	
		C				D
		00	01	11	10	

$$F = C + D'$$



$$F = (C'D)'$$

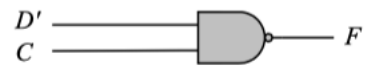



(b)

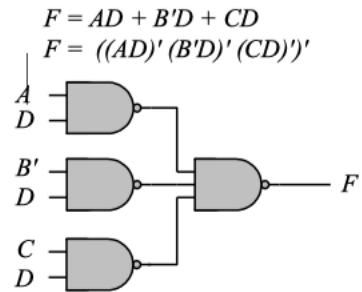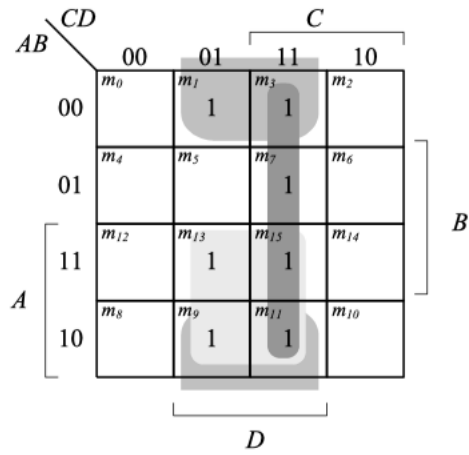

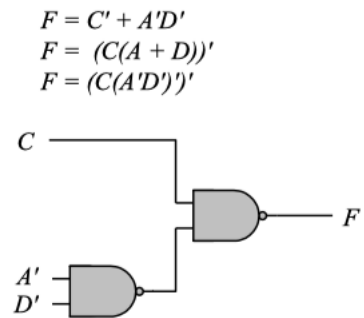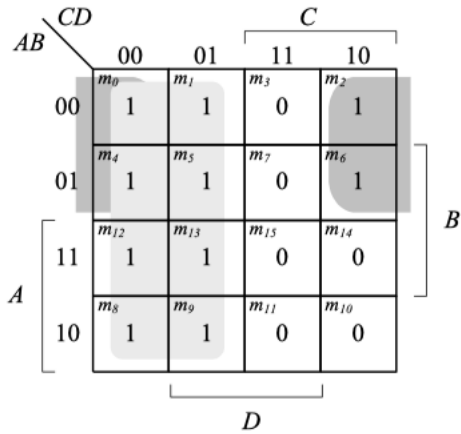(c) $F = (A' + C' + D')(A' + C')(C' + D')$
 $F' = (A' + C' + D')' + (A' + C')' + (C' + D')'$
 $F' = ACD + AC + CD$



(d)

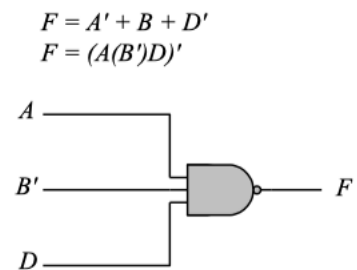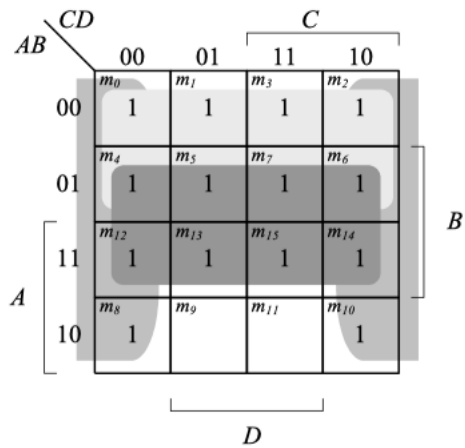

7) Draw a logic diagram using only two-input NOR gates to implement the following function:



$$F(A, B, C, D) = (A \oplus B)'(C \oplus D)$$

$$F = (A \oplus B)'(C \oplus D) = (AB' + A'B)'(CD' + C'D)$$

$$= (AB + A'B')(CD' + C'D) = ABCD' + ABC'D + A'B'CD' + A'B'C'D$$

$$F' = (AB + A'B')' + (CD' + C'D)'$$
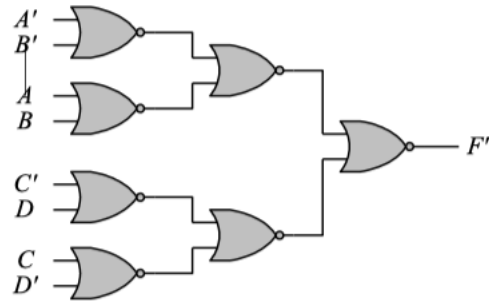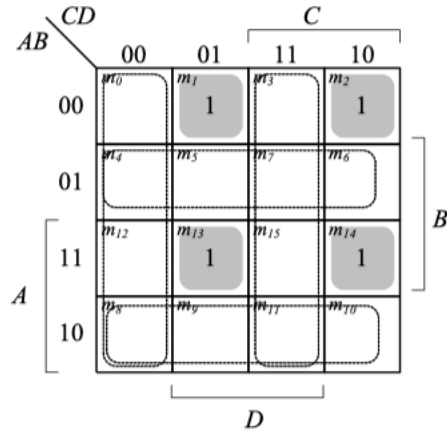
$$F' = ((A' + B)')' + ((A + B)')' + ((C' + D)')' + ((C + D)')'$$



Combinational Logic

- 8) Consider the combinational circuit shown in the following figure:

$$T_1 = B'C, T_2 = A'B, T_3 = A + T_1 = A + B'C,$$

$$T_4 = D \oplus T_2 = D \oplus (A'B) = A'BD' + D(A + B') = A'BD' + AD + B'D$$

$$F_1 = T_3 + T_4 = A + B'C + A'BD' + AD + B'D$$


$$\text{With } A + AD = A \text{ and } A + A'BD' = A + BD':$$

$$F_1 = A + B'C + BD' + B'D$$


$$\text{Alternative cover: } F_1 = A + CD' + BD' + B'D$$

$$F_2 = T_2 + D' = A'B + D'$$


ABCD	T ₁	T ₂	T ₃	T ₄	F ₁	F ₂
0000	0	0	0	0	0	1
0001	0	0	0	1	1	0
0010	1	0	1	0	1	1
0011	1	0	1	1	1	0
0100	0	1	0	1	1	1
0101	0	1	0	0	0	1
0110	0	1	0	1	1	1
0111	0	1	0	0	0	1
1000	0	0	1	0	1	1
1001	0	0	1	1	1	0
1010	1	0	1	0	1	1
1011	1	0	1	1	1	0
1100	0	0	1	0	1	1
1101	0	0	1	1	1	0
1110	0	0	1	0	1	1
1111	0	0	1	1	1	0

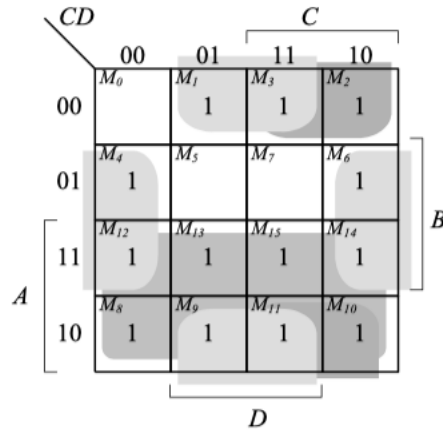

$$F_1 = A + B'C + B'D + BD'$$

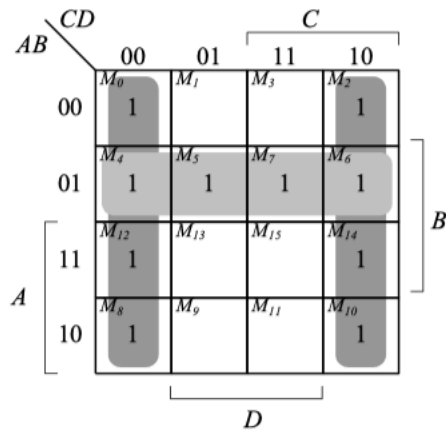


$$F_2 = A'B + D'$$

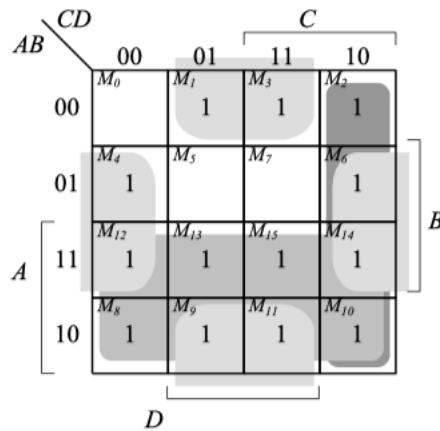

$$F_1 = A + CD' + B'D + BD'$$


- 9) Design a combinational circuit with three inputs, x , y , and z , and three outputs, A , B , and C . When the binary input is 0, 1, 2, or 3, the binary output is one greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is two less than the input.

xyz	ABC
000	010
001	011
010	100
011	101
100	001
101	010
110	011
111	100

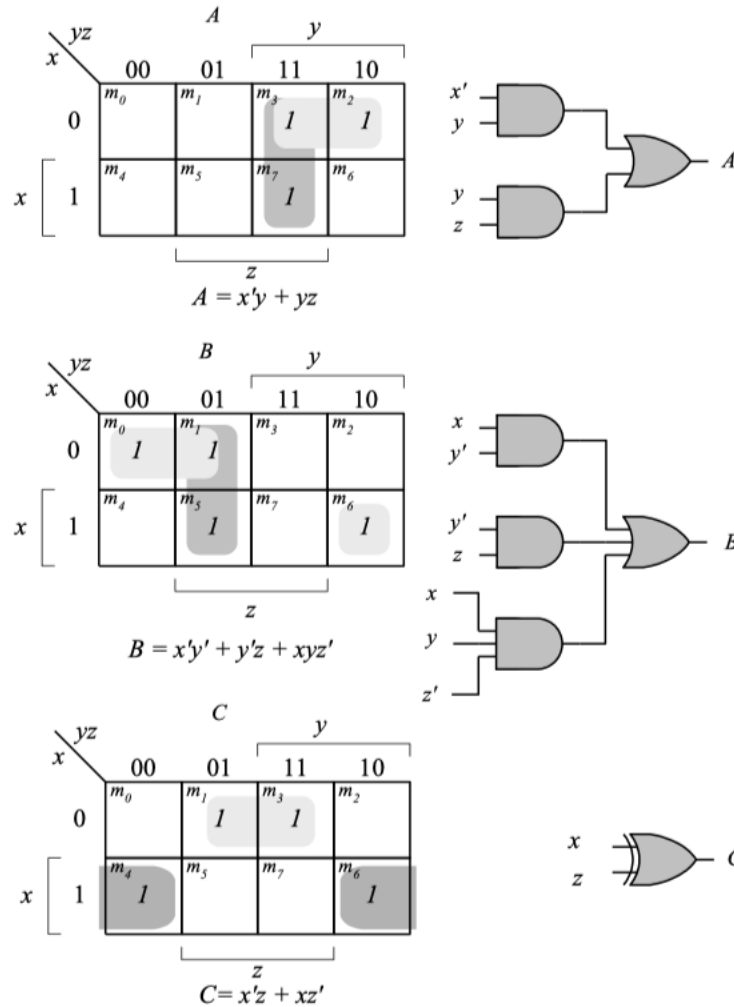


- 10) An BCD-to-seven-segment decoder is a combinational circuit that converts a decimal digit in BCD to an appropriate code for the selection of segments in an indicator used to display the decimal digit in a familiar form. The seven outputs of the decoder (a, b, c, d, e, f, g) select the corresponding segments in the display, as shown in Fig. (a). The numeric display chosen to represent the decimal digit is shown in Fig. (b). Using a truth table and Karnaugh maps, design the BCD-to-seven-segment decoder using a minimum number of gates. The six invalid combinations should result in a blank display. The following figure shows the segment designation and numbering scheme.


$ABCD$	a	b	c	d	e	f	g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

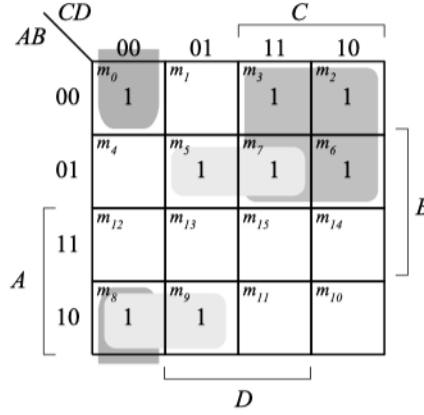


$$a = A'C + A'BD + B'C'D' + AB'C'$$

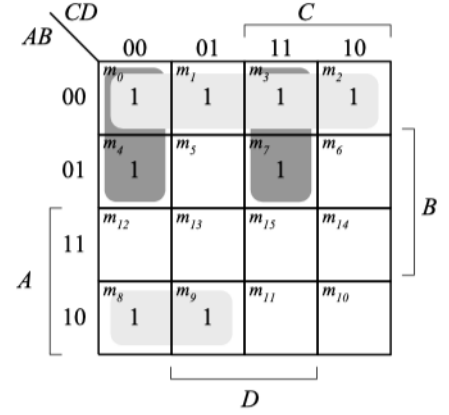


$$b = A'B' + A'C'D' + A'CD + AB'C'$$

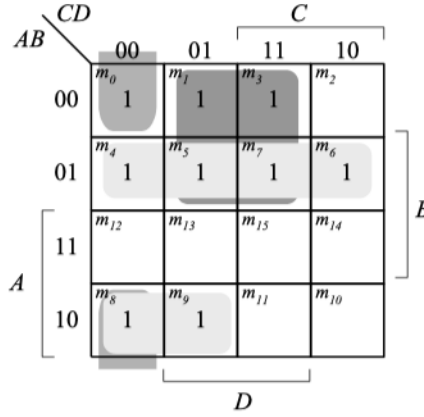


$$c = A'B + A'D + B'C'D' + AB'C'$$

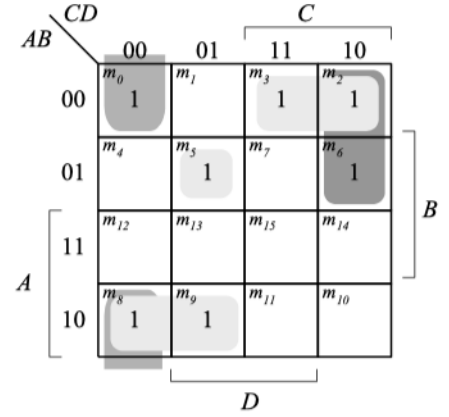

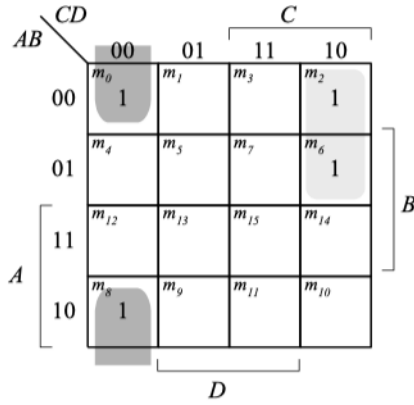
$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$



$$e = A'CD' + B'C'D'$$

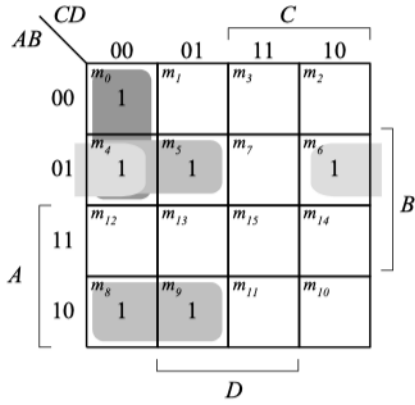



$$f = A'BC' + A'C'D' + A'BD + AB'C'$$

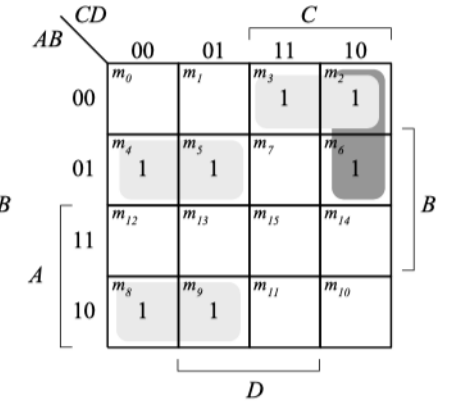

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$

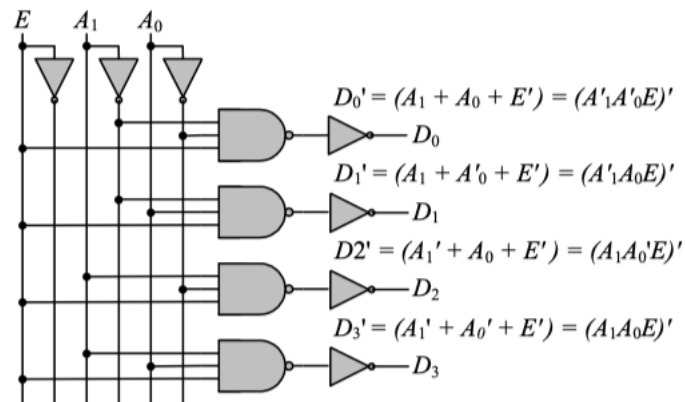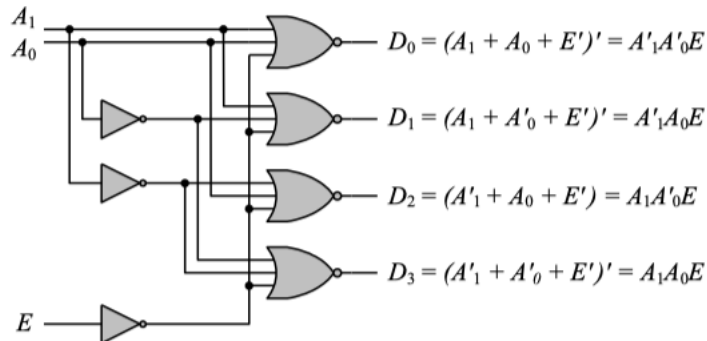11) Draw the logic diagram of a 2-to-4-line decoder using (a) NOR gates only and (b) NAND gates only. Include an enable input.

$$\begin{array}{ll} D_0 = A_1'A_0' = (A_1 + A_0)' & \text{(NOR)} & D_0' = (A_1'A_0')' & \text{(NAND)} \\ D_1 = A_1'A_0 = (A_1 + A_0')' & \text{(NOR)} & D_1' = (A_1'A_0)' & \text{(NAND)} \\ D_2 = A_1A_0' = (A_1' + A_0)' & \text{(NOR)} & D_2' = (A_1A_0')' & \text{(NAND)} \\ D_3 = A_1A_0 = (A_1' + A_0)' & \text{(NOR)} & D_3' = (A_1A_0)' & \text{(NAND)} \end{array}$$



12) A combinational circuit is specified by the following three Boolean functions:

