

2.1 Demonstrate the validity of the following identities by means of truth tables:

a) DeMorgan's theorem for three variables: $(x + y + z)' = x'y'z'$ and $(xyz)' = x' + y' + z'$

$$(x+y+z)' = x'y'z'$$

x	y	z	$(x+y+z)$	$(x+y+z)'$	x'	y'	z'	$x'y'z'$
0	0	0	0	1	1	1	1	1
0	0	1	1	0	1	1	0	0
0	1	0	1	0	1	0	1	0
0	1	1	1	0	1	0	0	0
1	0	0	1	0	0	1	1	0
1	0	1	1	0	0	1	0	0
1	1	0	1	0	0	0	1	0
1	1	1	1	0	0	0	0	0

∴ Since both columns are logically equivalent

$$(x+y+z)' = x'y'z'$$

$$(xyz)' = x' + y' + z'$$

x	y	z	xyz	$(xyz)'$	x'	y'	z'	$(x'+y'+z')$
0	0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	0	1
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	1
1	1	0	0	1	0	0	1	1
1	1	1	1	0	0	0	0	0

∴ Since both columns are logically equivalent

$$(xyz)' = (x'+y'+z')$$

∴ Since both columns are logically equivalent

$$x + yz = (x+y)(x+z)$$


e) $wxy'z + w'xz + wxyz$ to two literals

$$\begin{aligned}
 wxy'z + w'xz + wxyz &= wnz(y' + y) + w'nz \\
 &= wnz + w'nz \\
 &= nz(w + w') \\
 &= nz
 \end{aligned}$$

2.7 Draw logic diagrams of the circuits that implement the original and simplified expressions from 2.4 (c), (d), (e)


c) Original = $w'x(z' + y'z) + nz(w + w'y'z)$

Simplified = nz

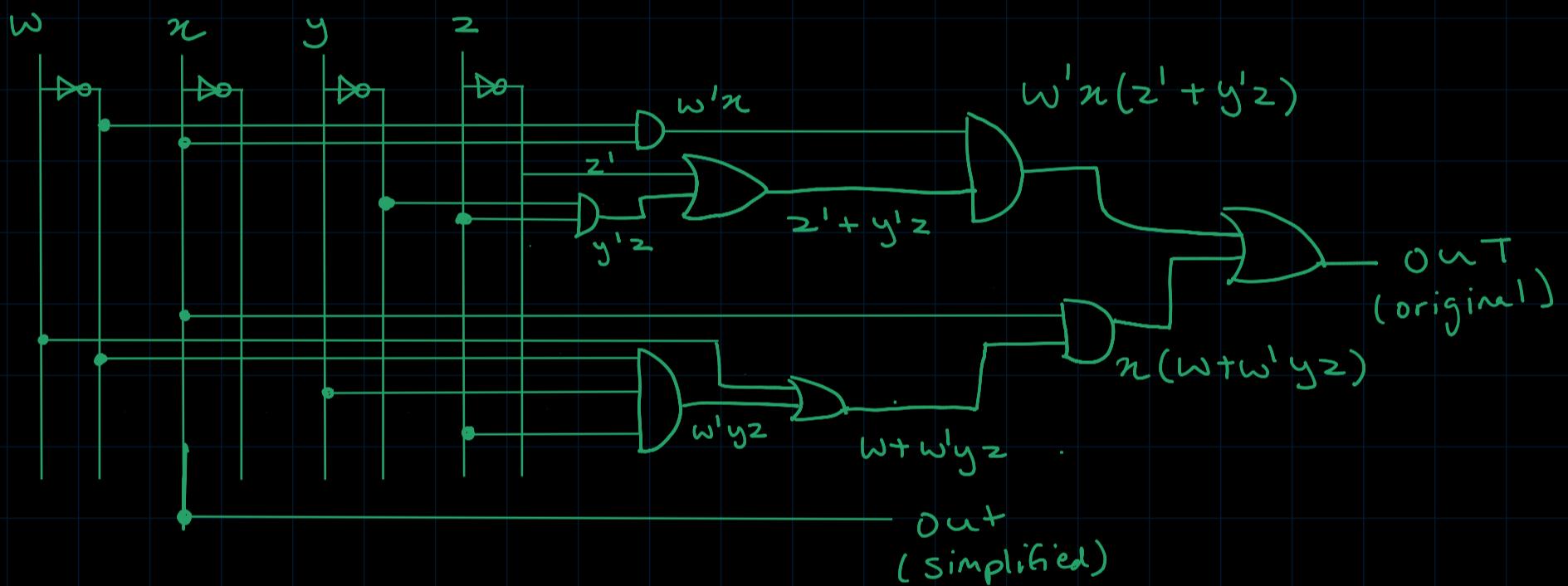

d) Original = $(w' + y)(w' + y')(w + x + y'z)$

Simplified = $w'(x + y'z)$

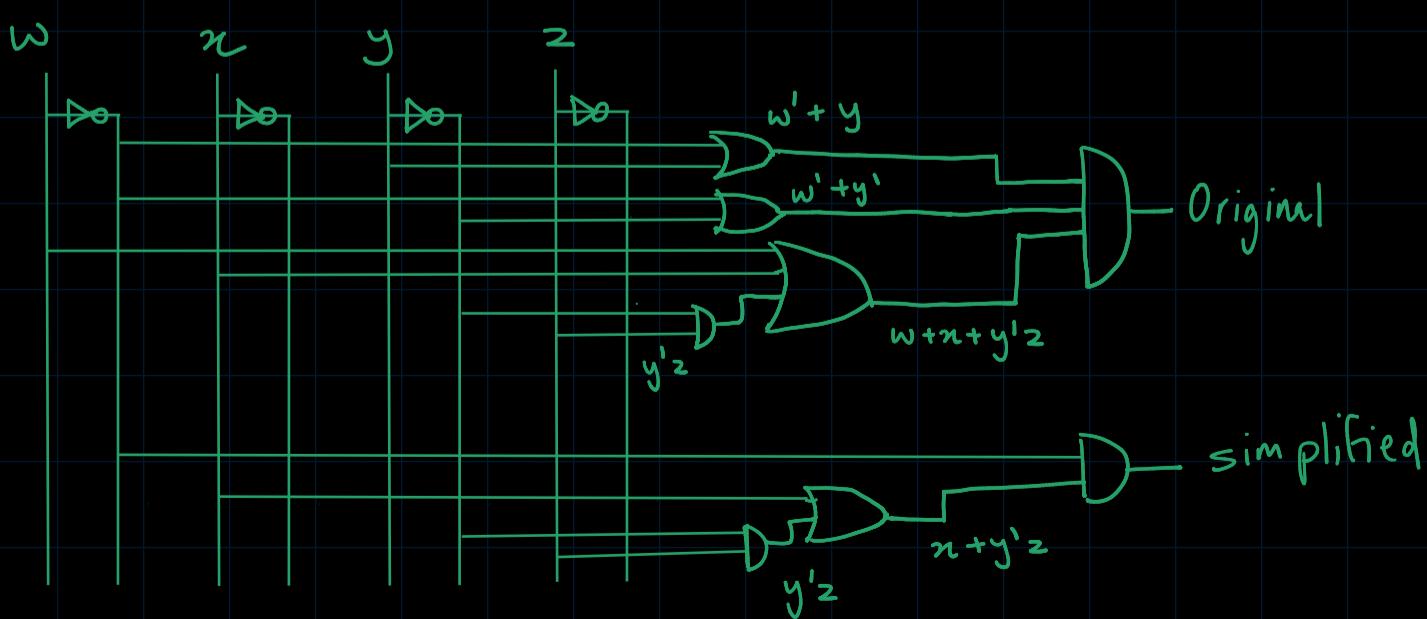

2.11 List the truth table of the function:

a) $F = xy + xy' + y'z$


x	y	z	xy	xy'	$y'z$	F
0	0	0	0	0	0	0
0	0	1	0	0	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	1	1	1
1	1	0	1	0	0	1
1	1	1	1	0	1	1

b) $F = ac + b'c'$


a	b	c	ac	$b'c'$	F
0	0	0	0	1	1
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	1	1
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	0	1

2.13 Draw Logic Diagrams to implement the following Boolean expressions:


a) $F = (u + x')(y' + z)$

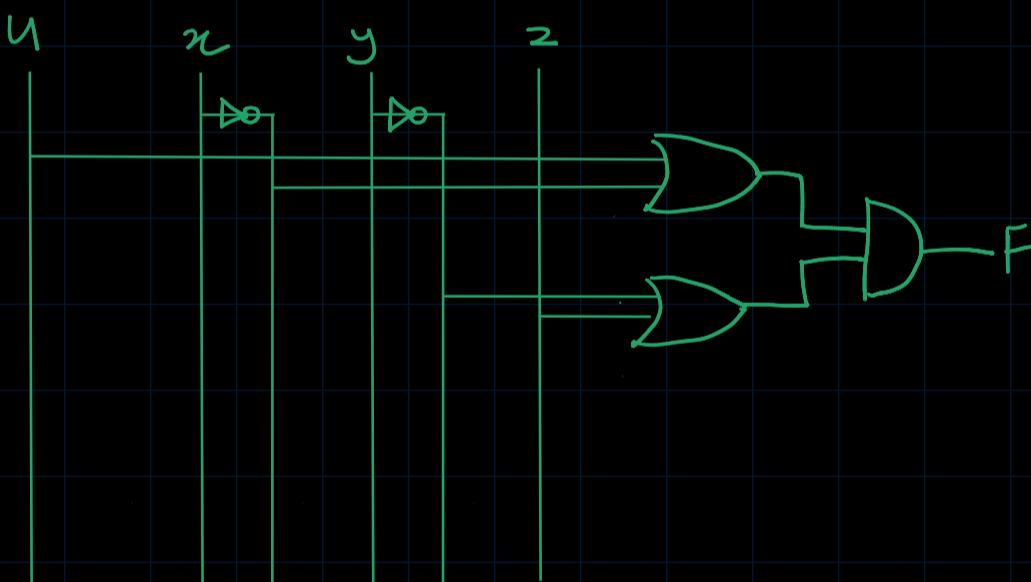


b) $F = (u \oplus y)' + x$

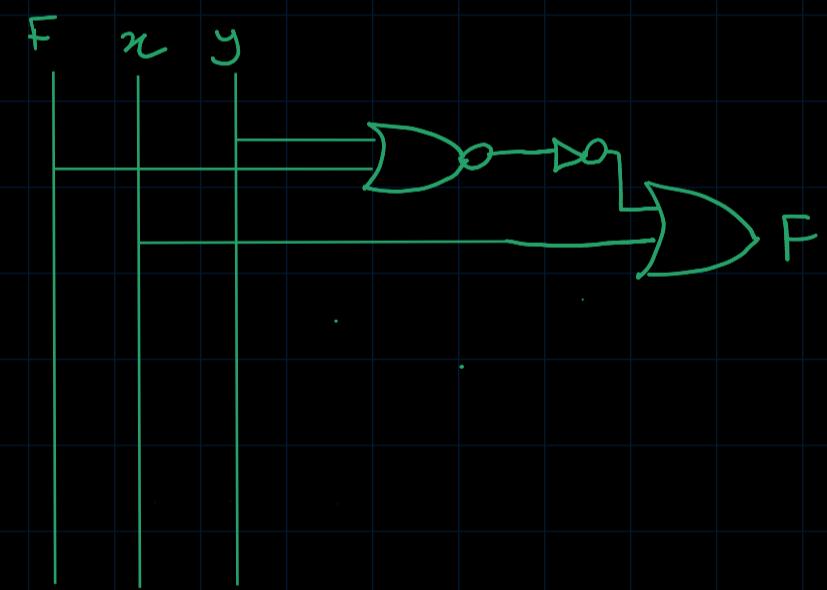


c) $F = (u' + x')(y + z')$

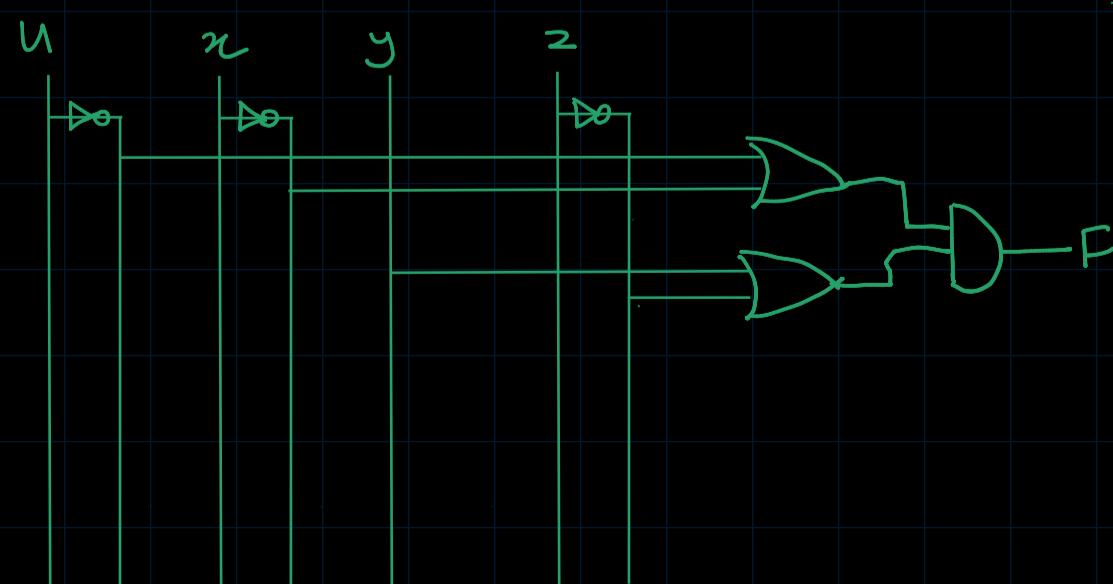


d) $F = u(x \oplus y) + y'$

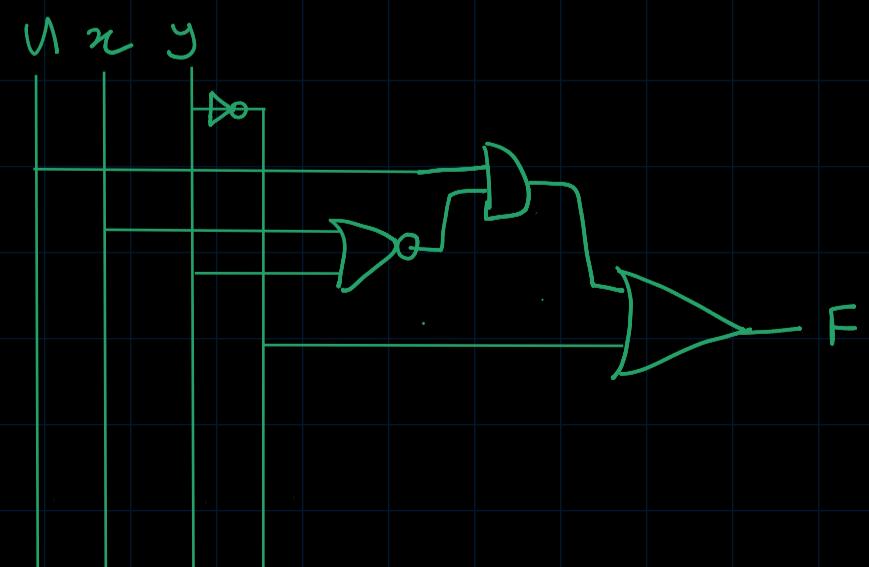

e) $F = U + YZ + UXU$

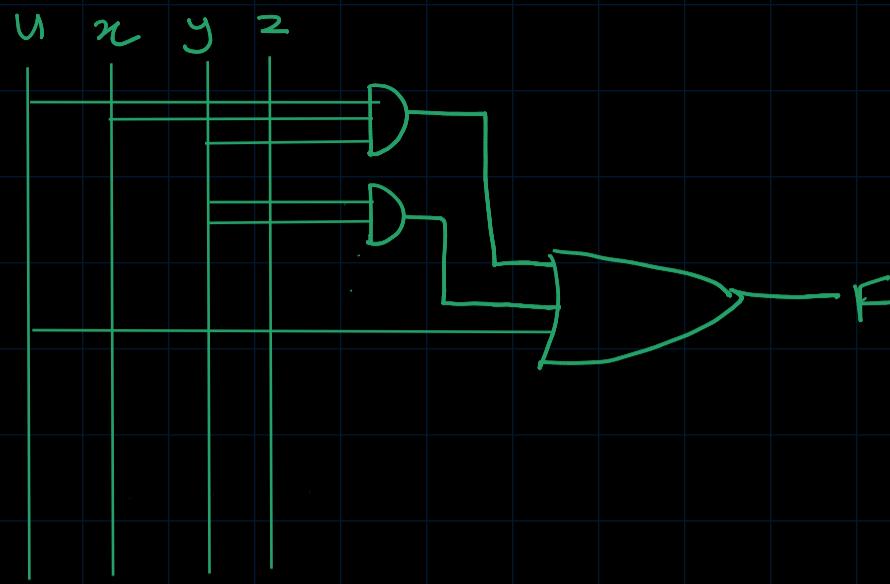


f) $F = U + X + X'(U + Y')$

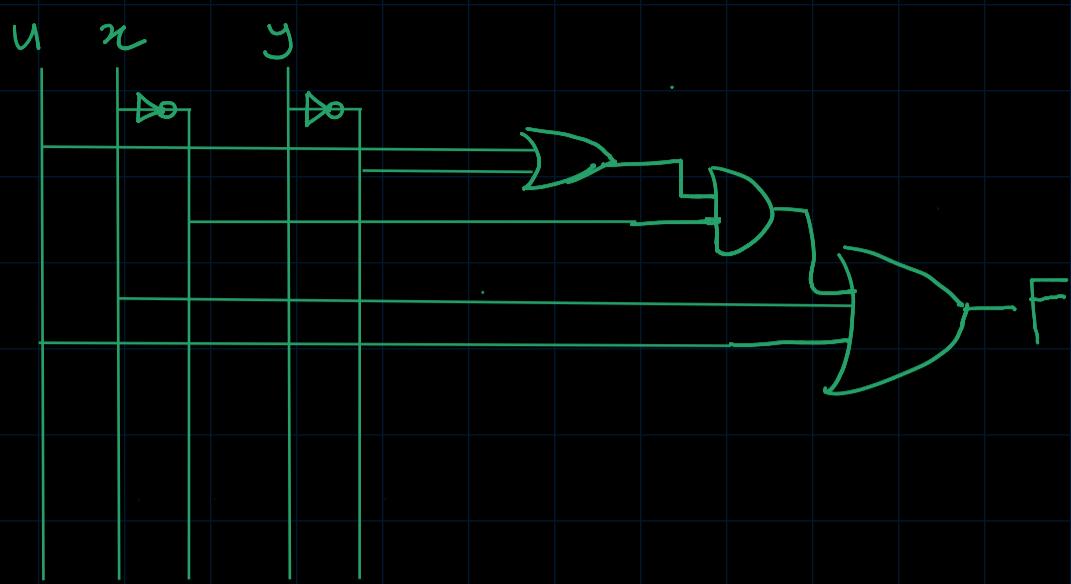

2.14 Implement the Boolean function $F = XY + X'Y' + Y'Z$


a) With AND, OR and inverter gates

$$F = XY + X'Y' + Y'Z$$

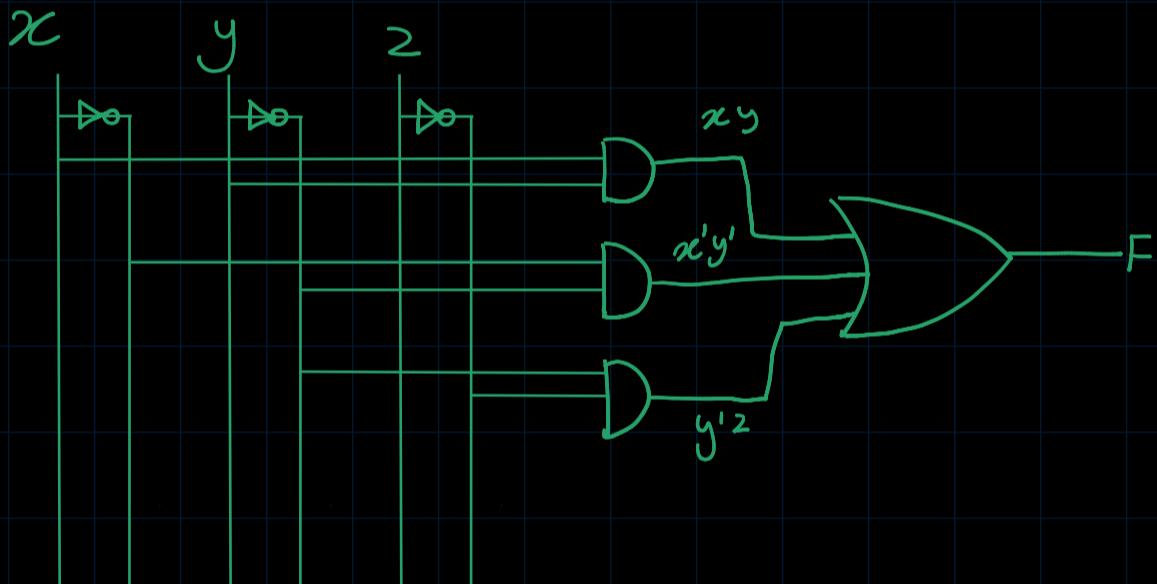

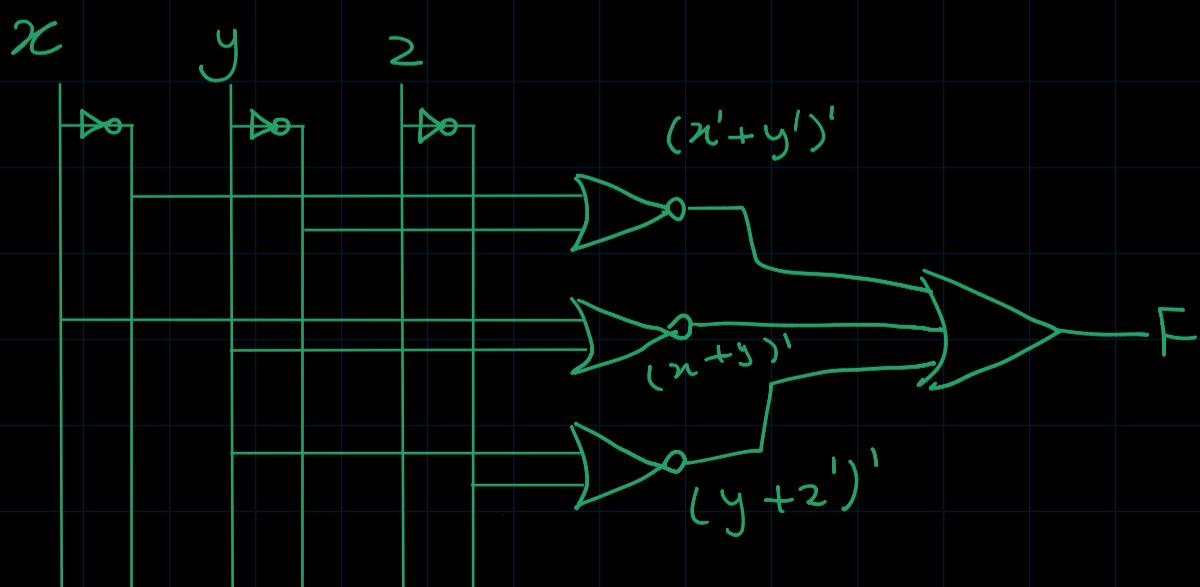
b) With OR and inverter gates

$$F = XY + X'Y' + Y'Z = (X' + Y')' + (X + Y)' + (Y + Z)'$$



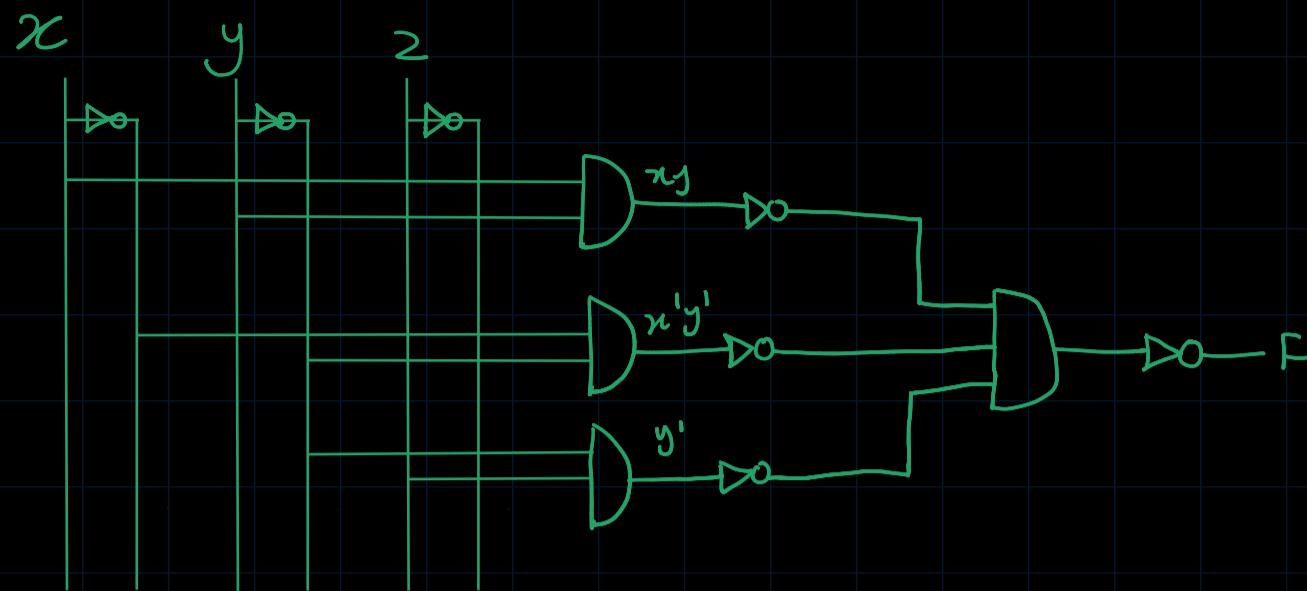
c) With AND and inverter gates

$$F = xy + x'y' + y'z = [(xy)'(x'y')'(y'z)']'$$



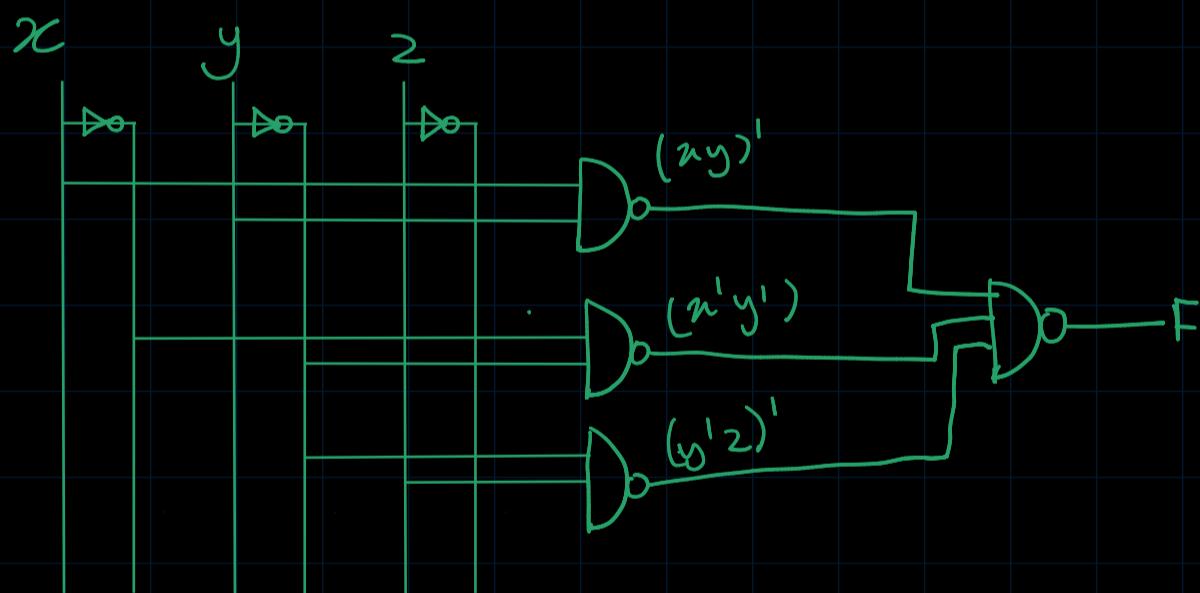
d) With NAND inverter gates

$$F = xy + x'y' + y'z = [(xy)'(x'y')'(y'z)']'$$



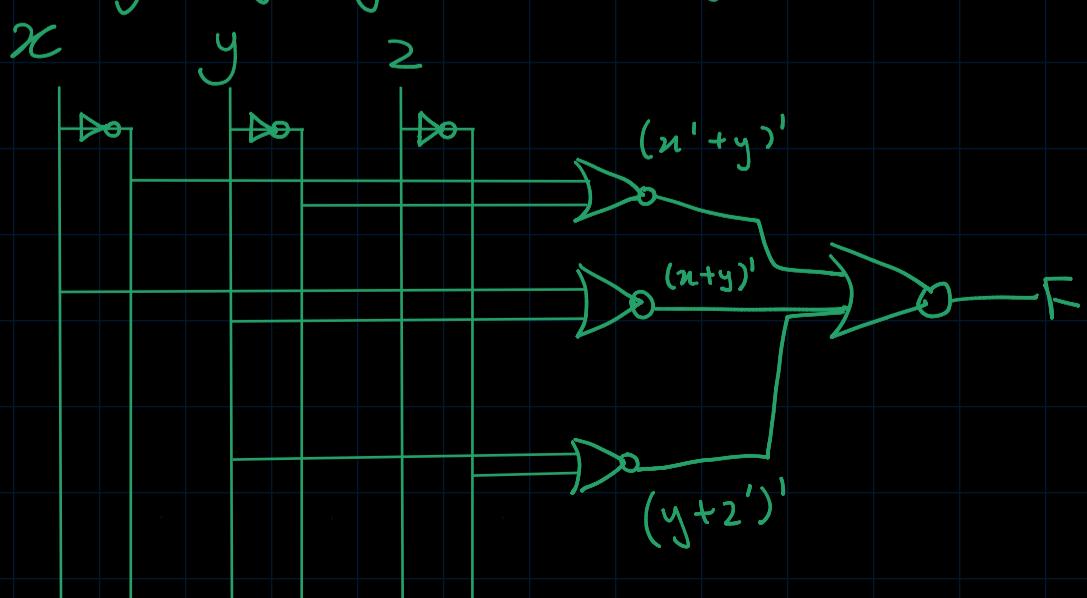e) With NOR and inverter gates

$$F = xy + x'y' + y'z = (x' + y')' + (x + y)' + (y + z)'$$




2.18 For the Boolean function

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

a) Obtain the truth table of F

w	x	y	z	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

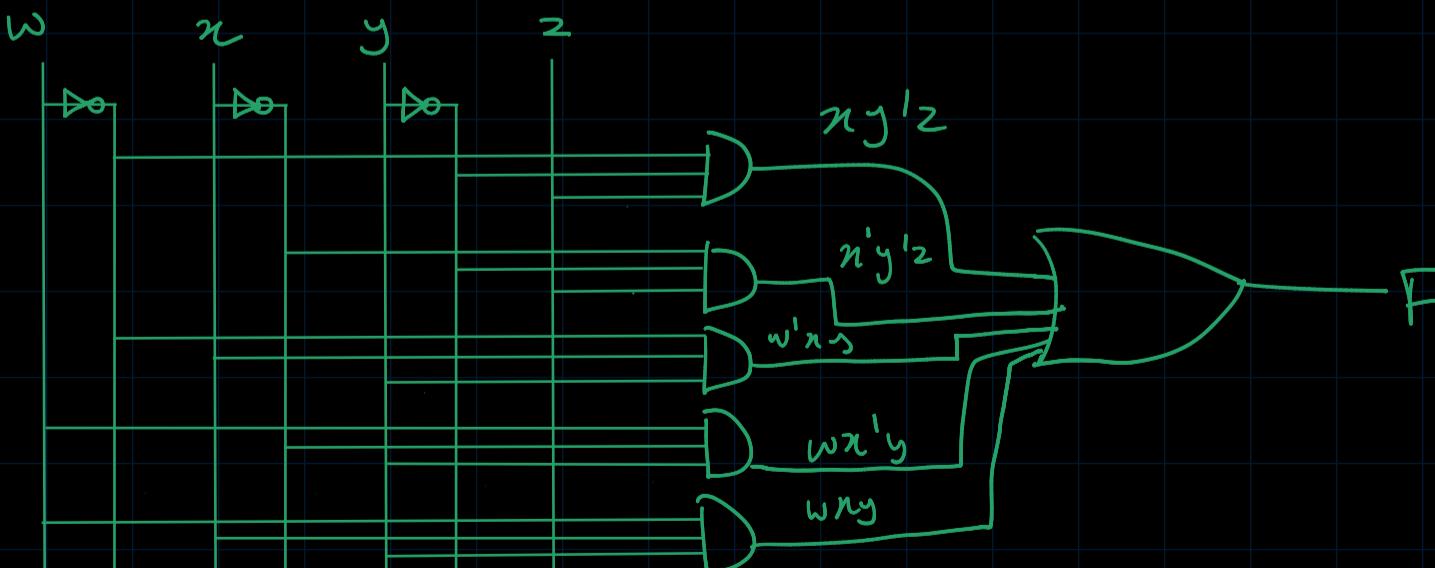b) Draw a logic diagram using the original Boolean Expression



c) Use Boolean algebra to simplify the function to a minimum number of literals

$$\begin{aligned}
 F &= \bar{w}y'z + w'y'z + \bar{w}y'ny + w\bar{n}'y + \bar{w}ny + w\bar{n}y \\
 &= y'z(w + \bar{w}) + ny(\bar{w} + w) + wy(\bar{n} + n) \\
 &= y'z + ny + wy \\
 &= y'z + y(n + w)
 \end{aligned}$$

d) Obtain the truth table of the function from the simplified expression and show it is the same as the one in part (a)

w	n	y	z	$y'z$	$n+w$	$y(n+w)$	F
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	1	1	0	1
0	1	1	0	0	1	1	1
0	1	1	1	0	1	1	1
1	0	0	0	0	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	0	1	1	1
1	0	1	1	0	1	1	1
1	1	0	0	0	1	0	0
1	1	0	1	1	1	0	1
1	1	1	0	0	1	1	1
1	1	1	1	0	1	1	1

