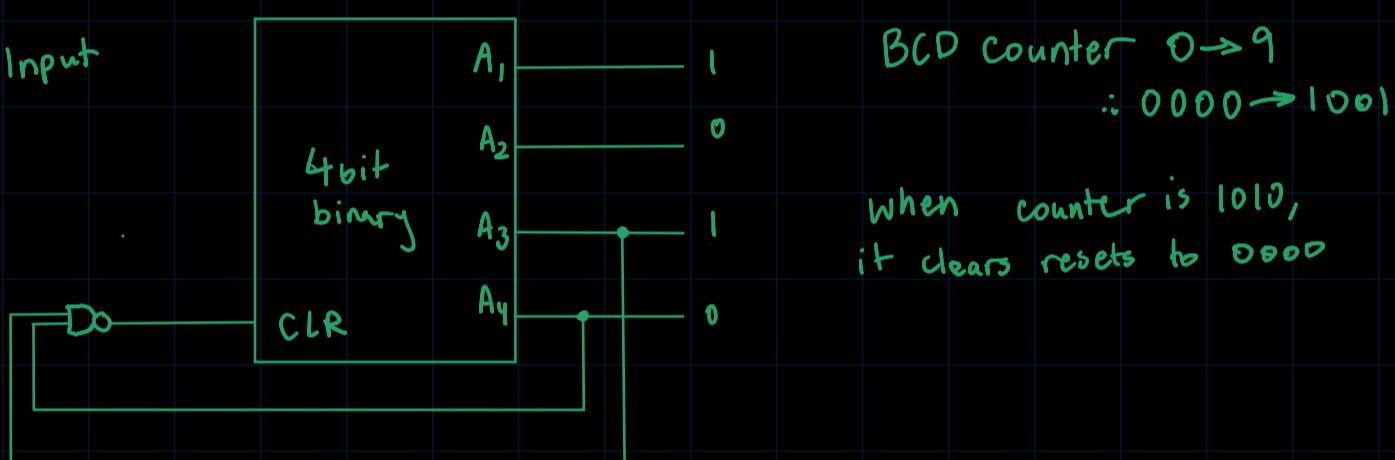


6.11 A ripple counter uses flip-flops that trigger on the positive edge of the clock. What will be the count if

- The normal outputs of the flip-flops are connected to the clock;
- The complement outputs of the flip-flops are connected to the clock?

- a) Count will be  $2^{n-1}$  where  $n$  is number of bits  
 b) Count will also be  $2^{n-1}$

6.13 Show that a BCD ripple counter can be constructed using a four-bit binary ripple counter with asynchronous clear and a NAND gate that detects the occurrence of count 1010.



6.19 The flip-flop input equations for a BCD counter using T flip-flops are given in Section 6.4. Obtain the input equations for a BCD counter that uses (a) JK flip-flop and (b) D flip-flops. Compare the three designs to determine which one is most efficient.

Present State	Next State	FF Inputs							
$A_1$ $A_2$ $A_3$ $A_4$	$A_1$ $A_2$ $A_3$ $A_4$	$J_{A1}$	$K_{A1}$	$J_{A2}$	$K_{A2}$	$J_{A3}$	$K_{A3}$	$J_{A4}$	$K_{A4}$
0 0 0 0	0 0 0 1	0	x	0	x	0	x	1	x
0 0 0 1	0 0 1 0	0	x	0	x	1	x	x	1
0 0 1 0	0 0 1 1	0	x	0	x	x	0	1	x
0 0 1 1	0 1 0 0	0	x	1	x	x	1	x	1
0 1 0 0	0 1 0 1	0	x	x	0	0	x	1	x
0 1 0 1	0 1 1 0	0	x	x	0	1	x	x	1
0 1 1 0	0 1 1 1	0	x	x	0	x	0	1	x
0 1 1 1	1 0 0 0	1	x	x	1	x	1	x	1
1 0 0 0	1 0 0 1	x	0	0	x	0	x	1	x
1 0 0 1	0 0 0 0	x	1	0	x	0	x	x	1

Present State	Next State	FF State
$A_1\ A_2\ A_3\ A_4$	$A_1\ A_2\ A_3\ A_4$	$D_{A1}\ D_{A2}\ D_{A3}\ D_{A4}$
0 0 0 0	0 0 0 1	0 0 0 1
0 0 0 1	0 0 1 0	0 0 1 0
0 0 1 0	0 0 1 1	0 0 1 1
0 0 1 1	0 1 0 0	0 1 0 0
0 1 0 0	0 1 0 1	0 1 0 1
0 1 0 1	0 1 1 0	0 1 1 0
0 1 1 0	0 1 1 1	0 1 1 1
0 1 1 1	1 0 0 0	1 0 0 0
1 0 0 0	1 0 0 1	1 0 0 1
1 0 0 1	0 0 0 0	0 0 0 0

Kmap for  $J_{A1}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$$J_{A1} = A_2 A_3 A_4$$

Kmap for  $K_{A1}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	0	1	x	x

$$K_{A1} = A_4$$

Kmap for  $J_{A2}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	0	0	1	0
01	x	x	x	x
11	x	x	x	x
00	0	0	x	x

$$J_{A2} = A_3 A_4$$

Kmap for  $K_{A2}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	x	x	x	x
01	0	0	1	0
11	x	x	x	x
00	x	x	x	x

$$K_{A2} = A_3 A_4$$

Kmap for  $J_{A3}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	0	1	x	x
01	0	1	x	x
11	x	x	x	x
00	0	0	x	x

$$J_{A3} = A_1 A_4$$

Kmap for  $K_{A3}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	x	x	1	0
01	x	x	1	0
11	x	x	x	x
00	x	x	x	x

$$K_{A3} = A_4$$

Kmap for  $J_{A4}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	1	x	x	1
01	1	x	x	1
11	x	x	x	x
00	1	x	x	x

$$J_{A4} = 1$$

Kmap for  $K_{A4}$

$A_3\ A_4$	00	01	11	10
$A_2\ A_1$	00	01	11	10
00	x	1	1	x
01	x	1	1	x
11	x	x	x	x
00	x	1	x	x

$$K_{A4} = 1$$

# of AND gates = 4

Total Gates = 4

$$J_{A1} = A_2 A_3 A_4$$

$$J_{A2} = A_3 A_4$$

$$J_{A3} = A_1 A_4$$


$$J_{A4} = 1$$

$$K_{A1} = A_4$$

$$K_{A2} = A_3 A_4$$

$$K_{A3} = A_4$$

$$K_{A4} = 1$$

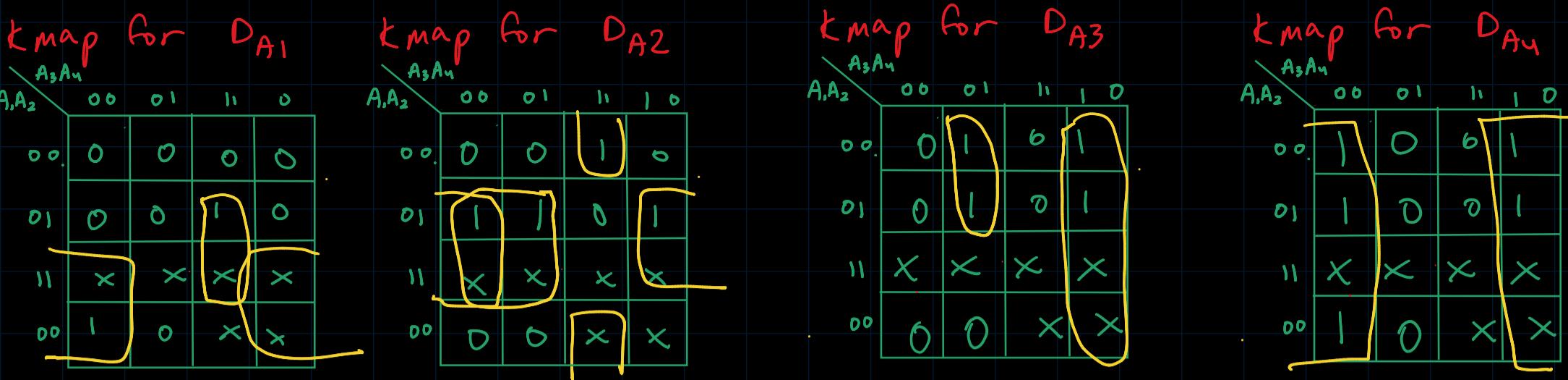

$$D_{A_1} = A_1 A_4' + A_2 A_3 A_4$$

$$D_{A_2} = A_2 A_3' + A_2 A_4' + A_4 A_2 A_1$$

$$= A_2 (A_3' + A_4') + A_2 A_3 A_4$$

$$= A_2 (A_3 A_4)' + A_2 (A_3 A_4)$$

$$= A_2 \oplus A_3 A_4$$

$$D_{A_3} = A_3 A_4' + A_1' A_3' A_4$$

$$D_{A_4} = A_1'$$

$$D_{A_1} = A_1 A_4' + A_2 A_3 A_4$$

$$D_{A_2} = A_2 \oplus A_3 A_4$$

$$D_{A_3} = A_3 A_4' + A_1' A_3' A_4$$

$$D_{A_4} = A_1'$$

# of AND gates = 5

# of OR gates = 2

# of XOR gates = 1

Total gates = 8 > 4

∴ JK is more efficient

## 6.27 Using JK Flip-flops:


a) Design a counter with the following repeated binary sequence

0, 1, 2, 3, 4, 5, 6


b) Draw the Logic Diagram of the counter

Present State	Next State	FF inputs
x y z	$x(t+1)$ $y(t+1)$ $z(t+1)$	$J_x$ $k_x$ $J_y$ $k_y$ $J_z$ $k_z$
0 0 0	0 0 1	1 0 X 0 X 1 X
0 0 1	0 1 0	0 0 X 1 X X 1
0 1 0	0 1 1	1 0 X X 0 1 X
0 1 1	1 0 0	0 1 X X 1 X 1
1 0 0	1 0 1	1 X 0 0 X 1 X
1 0 1	1 1 0	0 X 0 1 X X 1
1 1 0	0 0 0	0 X 1 X 1 0 X
1 1 1	X X X	X X X X X X X


Kmap for  $J_x$

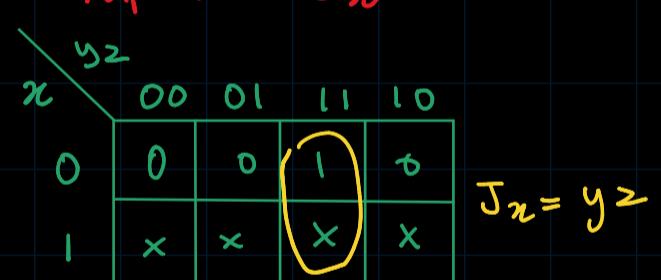

Kmap for  $J_y$

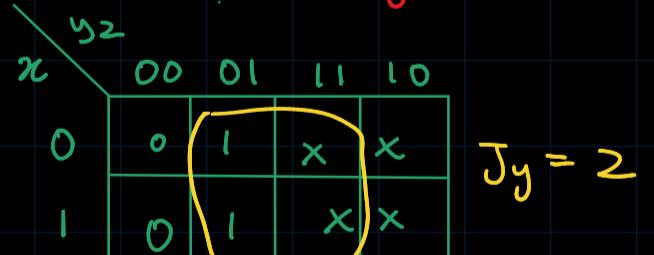


Kmap for  $J_z$

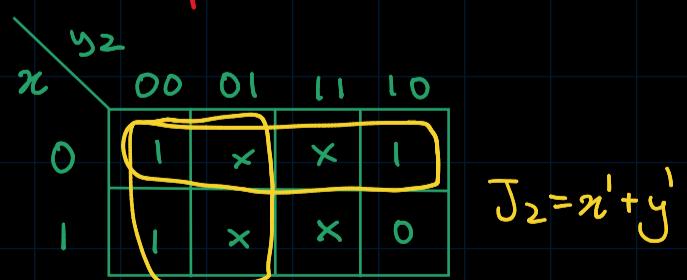


Kmap for  $k_x$



Kmap for  $k_y$

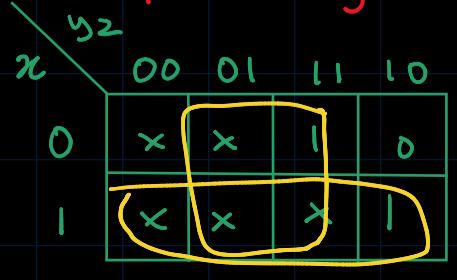

Kmap for  $k_z$

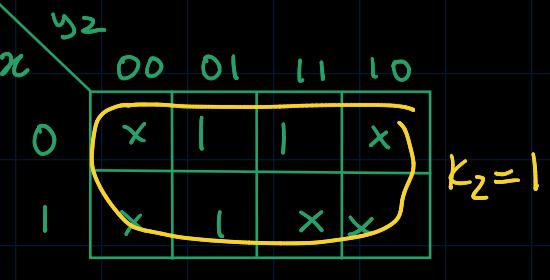

Present State	Next State	FF inputs
$x \ y \ z$	$x(t+1) \ y(t+1) \ z(t+1)$	$J_x \ k_x \ J_y \ k_y \ J_z \ k_z$
1 1 1	0 0 0	0 1 1 1 1 0 1

