 



Synchronous Sequential Logic

- 1) The D latch of Fig. 5.6 is constructed with four NAND gates and an inverter. Consider the following three other ways for obtaining a D latch. In each case, draw the logic diagram and verify the circuit operation.


(a)




(b)

 


(c)

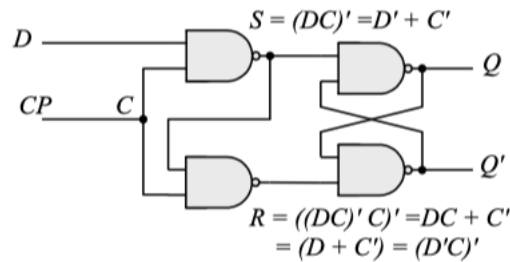

 - 2) Construct a JK flip-flop using a D flip-flop, a two-to-one-line multiplexer, and an inverter.



 - 3) A sequential circuit with two D flip-flops A and B, two inputs, x and y; and one output z is specified by the following next-state and output equations:



(b)


$$A(t+1) = xy' + xB$$

$$B(t+1) = xA + xB'$$

$$z = A$$

Present state		Inputs		Next state		Output
A	B	x	y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	1	1	1
1	0	1	1	1	1	1
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

(c)

 

- 4) A sequential circuit has two JK flip-flops A and B and one input x. The circuit is described by the following flip-flop input equations:

Answer of (a) on the left, and the answer of (b) on the right:


$$J_A = x \quad K_A = B$$

$$J_B = x \quad K_B = A'$$

$$A(t+1) = J_A A' + K_A' A = xA' + B'A$$

$$B(t+1) = J_B B' + K_B' B = xB' + AB$$

x	A	B	$xA' + B'A$	$xB' + AB$
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

 



- 5) A sequential circuit has two JK flip-flops A and B, two inputs x and y, and one output z. The flip-flop input equations and circuit output equation are

$$\begin{aligned} \text{(a)} \quad J_A &= Bx + B'y' & J_B &= A'x \\ K_A &= B'xy' & K_B &= A + xy' & z &= Axy + Bx'y' \end{aligned}$$

(b)

Present state		Inputs		Next state		Output	FF Inputs			
A	B	x	y	A	B	z	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	1	0	1	1	1	1
0	0	1	1	0	1	0	0	0	1	0
0	1	0	0	0	1	1	0	0	0	0
0	1	0	1	0	1	0	0	0	0	0
0	1	1	0	1	0	0	1	0	1	0
0	1	1	1	1	1	0	1	0	1	0
1	0	0	0	1	0	0	1	0	0	1
1	0	0	1	1	0	0	0	0	0	1
1	0	1	0	0	0	0	1	1	0	1
1	0	1	1	1	0	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1
1	1	0	1	1	0	0	0	0	0	1
1	1	1	0	1	0	0	1	0	0	1
1	1	1	1	1	0	1	1	0	0	1

(c)

  


Registers and Counters

- 6) Draw the logic diagram of a four-bit register with four D flip-flops and four 4×1 multiplexers with mode selection inputs s_1 and s_0 . The register operates according to the following function table.

Stage of register: (s_1, s_0): (0,0) – no change, (1,0) – complement outputs
 (0,1) – Synchronous clear, (1,1) = Load parallel data.


Stage logic diagram:

 

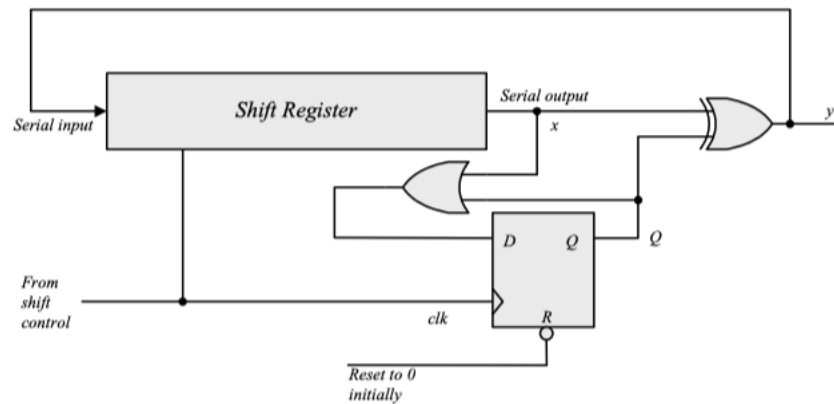- 7) Design a serial 2's complementer with a shift register and a flip-flop. The binary number is shifted out from one side and it's 2's complement shifted into the other side of the shift register.

Note that $y = x$ if $Q = 0$, and $y = x'$ if $Q = 1$. Q is set on the first 1 from x .

Note that $x \oplus 0 = x$, and $x \oplus 1 = x'$.



- 8) A binary ripple counter uses flip-flops that trigger on the positive-edge of the clock. What will be the count if:

Answer:

(a) A count down counter.

(b) A count up counter.

- 9) A digital system has a clock generator that produces pulses at a frequency of 80 MHz. Design a circuit that provides a clock with a cycle time of 50 ns.

- 10) Using JK flip flops, design a counter with the following repeated binary sequence: 0, 1, 2, 3, 4, 5, 6.

Present state	Next state	Flip-flop inputs					
<i>ABC</i>	<i>ABC</i>	J_A	K_A	J_B	K_B	J_C	K_C
000	001	0	x	0	x	1	x
001	010	0	x	1	x	x	1
010	011	0	x	x	0	1	x
011	100	1	x	x	1	x	1
100	100	x	x	0	0	1	x
101	110	x	x	1	x	x	1
110	000	x	x	x	1	0	x
111	xxx	x	x	x	x	x	x

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	m_0	m_1	m_3 1	m_2
	1	m_4 x	m_5 x	m_7 x	m_6 x

$$J_A = BC$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	m_0 x	m_1 x	m_3 x	m_2 x
	1	m_4	m_5	m_7 x	m_6 1

$$K_A = B$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	m_0	m_1 1	m_3 x	m_2 x
	1	m_4	m_5 1	m_7 x	m_6 x

$$J_B = C$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	m_0 x	m_1 x	m_3 1	m_2
	1	m_4 x	m_5 x	m_7 x	m_6 1

$$K_B = A + C$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	m_0 1	m_1 x	m_3 x	m_2 1
	1	m_4 1	m_5 x	m_7 x	m_6

$$J_C = A' + B'$$

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	m_0 x	m_1 1	m_3 1	m_2 x
	1	m_4 x	m_5 1	m_7 x	m_6 x

$$K_C = 1$$